

Inductors

Definitions

Inductors

Inductors produce magnetic fields when current is **changing** within the coil. They oppose **any change** in current (either an increase or a decrease). This **opposition** is non-linear (just like capacitors)

Y represents what would happen to the current without an inductor, X with an inductor.

The **time constant**, τ , for this circuit is when I reaches 63% of maximum I.

The curve can be explained using Lenz's law and the creation of a back EMF. The EMF (Voltage) created by the inductor is in the opposite direction to the voltage that made it.

Equations

$\mathcal{E} = -L \frac{\Delta I}{\Delta t}$	EMF	\mathcal{E}	V
	Inductance	L	H
	Current	I	A
$E = \frac{1}{2} LI^2$	Energy	E	J
	Inductance	L	H
$\tau = \frac{L}{R}$	Time constant	τ	s
	Inductance	L	H
	Resistance	R	Ω

Questions

ELECTROMAGNETISM (2022;2)

David uses a 1.60 H, 22.0 Ω inductor, and connects it to a 12.0 V power supply. The inductor can be considered as a pure inductor in series with a resistor, as shown in the diagram.

- Calculate the circuit current after two time constants, once the switch is closed and current begins to flow.
- State the voltage across the pure inductor **and** the voltage across the resistor once the current is steady.
- Once the current has reached a steady value, the switch is opened, and current falls to zero in 2.50×10^{-2} s. Calculate the size of the average induced voltage. State the direction of the induced voltage across the inductor.
- The 22.0 Ω resistor is replaced with a 44.0 Ω resistor, and the switch is then closed. Explain, by comparing quantitatively (how much), the changes that will take place for:
 - the size of the maximum current drawn from the circuit
 - the time constant
 - the energy stored in the inductor once the current is steady.

Terms

Tips

- An inductor is regarded to have a stable magnetic field or no magnetic field after $5 \times \tau$ (although theoretically this never happens)

Answers


(a) $I_{\max} = \frac{V_s}{R} = \frac{12.0}{22.0} = 0.545 \text{ A}$
 Current after two time constants = $I = I_{\max}(1 - e^{-2})$
 $I = 0.545(1 - e^{-2}) = 0.471 \text{ A}$

(b) $V_L = 0, V_R = 12 \text{ V}$

(c) Voltage opposes the change in current, it will try to prevent the current from decreasing and so will act in the same direction as the source voltage.

$V = \frac{L \Delta I}{t}$
 $I = \frac{V}{R} = \frac{12.0}{22.0} = 0.545 \text{ A}$
 $V = \frac{1.60 \times 0.545}{2.50 \times 10^{-2}} = 34.9 \text{ V}$

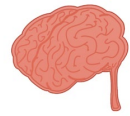(d) If the resistance was changed to 44.0 Ω , then the size of the maximum current once it was steady would halve, since $I = V/R$. The increased resistance will have an effect on the time constant as $\tau = L/R$, so time constant would halve. Hence it will take less time for the current to become steady. Since the energy stored in the inductor $E_p = \frac{1}{2} LI^2$, and the current has halved, the energy stored in the inductor once the current is steady would be $\frac{1}{4}$.



$\varepsilon = -L \frac{\Delta I}{\Delta t}$	EMF	ε	V
	Inductance	L	H
	Current	I	A
	Time	t	s
$E = \frac{1}{2} LI^2$	Energy	E	J
	Inductance	L	H
	Current	I	A
$\tau = \frac{L}{R}$	Time constant	τ	s
	Inductance	L	H
	Resistance	R	Ω