

Things to remember in the last hour before the exam: Level 3 Electricity

(This is not a revision sheet – you’ve done that by now - it’s a list of things you might want to memorise at the last minute...)

- | | | |
|--|--------------------------------------|--|
| | Useful data | |
| | Speed of light | $= 3.00 \times 10^8 \text{ m s}^{-1}$ |
| | Charge on the electron | $= -1.60 \times 10^{-19} \text{ C}$ |
| | Acceleration due to gravity on Earth | $= 9.81 \text{ m s}^{-2}$ |
| | Permittivity of free space | $= 8.85 \times 10^{-12} \text{ F m}^{-1}$ |
| | Universal gravitational constant | $= 6.67 \times 10^{-11} \text{ N m}^2 \text{ kg}^{-2}$ |
1. Most equations are only used once so highlight an equation once you have used it (but $V=IR$ will probably be used more than once). Any constants you need e.g. $e = -1.6 \times 10^{-19} \text{ C}$ will be given to you e.g.
 2. You must convert quantities into **SI** before using them in an equation (e.g. $5 \text{ mC} = 5 \times 10^{-3} \text{ C}$) Remember prefixes ($n = 10^{-9}$, $\mu = 10^{-6}$, $m = 10^{-3}$, $c = 10^{-2}$, $k = 10^3$, $M = 10^6$, $G = 10^9$)
 3. If you can’t remember the units, use the units on the other side of the equation e.g. $\epsilon_0 = \text{Cd/A}$ so absolute permittivity, ϵ_0 has units of $\text{F (from C)} \times \text{m (from d)} \div \text{m}^2 \text{ (from A)}$ i.e. F m^{-1}
 4. If you are asked to give the answer to the correct number of significant figures use the information in the question (the least number of significant figures) and write your rounded answer after your calculated answer (and not instead of) – have a guess if you can’t remember and it isn’t the same rule as Chemistry – you will probably only be asked once if at all
 5. Remember the basic electricity rules (in a series circuit I is the same but V splits; in a parallel circuit V is the same but I splits). You might need to use $R_T = R_1 + R_2$ is for adding resistors in series, $1/R_T = 1/R_1 + 1/R_2$ is for adding resistors in parallel (but probably not)
 6. You may need to use $\epsilon = V + Ir$ – memorise this and write it down as soon as you are allowed to in the exam
 7. The terminal p.d. $V = \text{EMF} - \epsilon$ **only** when $I = 0$ because the load resistor R is very large/or the is an open switch
 8. Ir is the lost volts (more lost volts the hotter the battery is and the more inadequate it becomes)
 9. You might need to use $C_T = C_1 + C_2$ is for adding capacitors in **parallel**, $1/C_T = 1/C_1 + 1/C_2$ is for adding capacitors in **series** (they are insulators and therefore the opposite to resistors)
 10. Kirchhoff’s laws – sum of voltages in a loop are zero (law of conservation of energy), current entering a junction = current leaving a junction (law of conservation of charge)
 11. If you need to solve a Kirchhoff’s law question by simultaneous equations something has gone terribly wrong – back up and check if one of the currents was zero because the *current was going through a voltmeter ($I \approx 0$ because R is soooo big)*
 12. In the Impedance question, remember R is resistance, X_c reactance of the capacitor and X_L reactance of the inductor
 13. Z (Impedance) = R “at resonance” (when $f = f_0$) and then I is the maximum value
 14. Capacitors block low frequency and inductors block high frequency
 15. X_c and X_L are 180° out of phase
 16. A phasor diagram is like a vector diagram – it doesn’t have to be used in a reference circle
 17. Reactance X_c and X_L have units of Ω
 18. ELI the ICEman might be the key to phasor diagrams (or whatever your teacher told you)
 19. $\omega = 2\pi f$ where f is the frequency of the supply voltage e.g. **50 Hz** ($\omega = 314 \text{ s}^{-1}$)
 20. If it asks you to explain something (e.g. “Describe what happens to the current flowing through a $100 \mu\text{F}$ capacitor if the frequency of the supply is doubled.”) Don’t be afraid to put in numbers to the equation twice e.g. $I = V/X_c$ so $I = V \times 2\pi f$ using two different values of f and then write a comparison of your answers
 21. Leave *show that the resonant frequency equals....* until the end of the exam if it turns up

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$f_0 = \frac{1}{2\pi} \sqrt{\frac{1}{LC}}$$